

Note: NO DOUBTS!! (If required, make and state your assumptions)

Q1. Using postulates of Boolean algebra and the theorems, prove $BC + A'B' + A'C' = ABC + A'$ [2 marks]

Q2. Following pairs of 8-bit vectors x and y representing integers in the two's complement system.

(a) $X=10110110$ $Y=01100111$

(b) $X=10101010$ $Y=11110001$

Obtain the $(x+y)$ and $(x-y)$ using two's complement arithmetic? Also describe the values of conditions OVF (Over flow), ZERO, SIGN? [2 marks]

Q3. With a suitable example, explain how a buffer can be used to reduce the propagation delay of a gate network? [2 marks]

Q4. A combinational system has four inputs a, b, c, d and one output y . The output y is 1 if and only if the number represented by (a, b, c, d) in binary code is prime. Design a minimal two-level network to implement this system, using Quine-McCluskey minimization method (0 and 1 are not prime). [6 marks]

Q5. For a sequential system described using the given state table description

(a) Determine the minimal state table and draw the state diagram? [4 marks]

(b) Design the sequential system for the minimised state description using JK Flipflop? [6 marks]

PS	x=a	x=b	x=c	x=d
A	D,1	C,0	B,1	F,1
B	C,0	F,1	E,1	B,0
C	B,1	A,0	D,1	F,1
D	G,0	F,1	E,1	B,0
E	C,0	A,1	D,1	E,0
F	C,1	F,1	D,0	H,0
G	D,1	A,0	B,1	F,1
H	B,1	C,0	B,1	F,1
NS, z				

(PS: Present state, NS: Next State)


Q6. Implement the following function using cascade network [2+2 marks]

$F(a, b, c, d) = \text{one-set } (1, 3, 6, 7, 9, 11, 14)$

(a) of Multiplexers (4:1) (b) of decoder (2:4) and one OR gate

Q7. Compare two different approaches (coincident and tree decoding) of decoder network in terms of resources, delay, and load factor at input and output side? [4 marks]

 Q8. A 4-bit right shift register is initialized to values 1000 for (Q_0, Q_1, Q_2, Q_3) . The input (D) to the register is derived from Q_0, Q_2 , and Q_3 as shown in the figure. Write down the sequence generated by the circuit till its repetition? [2 marks]



Q9. Design a sequential system which has an input $I \in \{0,1\}$ and produces output $z=1$ when pattern (101011) occurs five times. (Hint: Design the system in two modules: pattern recognizer and counter) [4 marks]

Q10. Design a network using Modulo-8 binary counter, decoder and SR flipflop to produce the different timing signals with different duty cycles? [4 marks]

(a) duty cycle= 25% (b) duty cycle=75%

Q11. For the given function design the simple execution graph and explain how it can be modified to reduce the cost of system and to reduce the timing parameters? [5 marks]

```
While{
    Read a, b, c, d, x
    Z1=a+b+c+d
    If(x=0)
    {
        Z2=(a+b)*c
    }
    Else
    {
        Z2=(a+b)*(c+d)
    }
}
```