

# Digital Circuits and Systems

## Mid Semester Exam-II

Date: 1<sup>st</sup> October 2014

Time: 60 Minutes


Max Marks. 15

Notes: All questions are compulsory.

Marks of each question are mention against it.

Assumptions made should be written clearly.

**1:** Consider number A of X bits stored in sign magnitude as shown in the figure 1 below (most significant bit is the sign, remaining X-1 bits magnitude). We want to multiply A with 2. Design the digital circuit that can inform us (by turning a light on) if the result could still be stored in the X-1 bits (i.e., no overflow would result). You can assume that in your design you may use “wires” connected directly to the bit locations. Use the MINIMUM number of gates. [5]

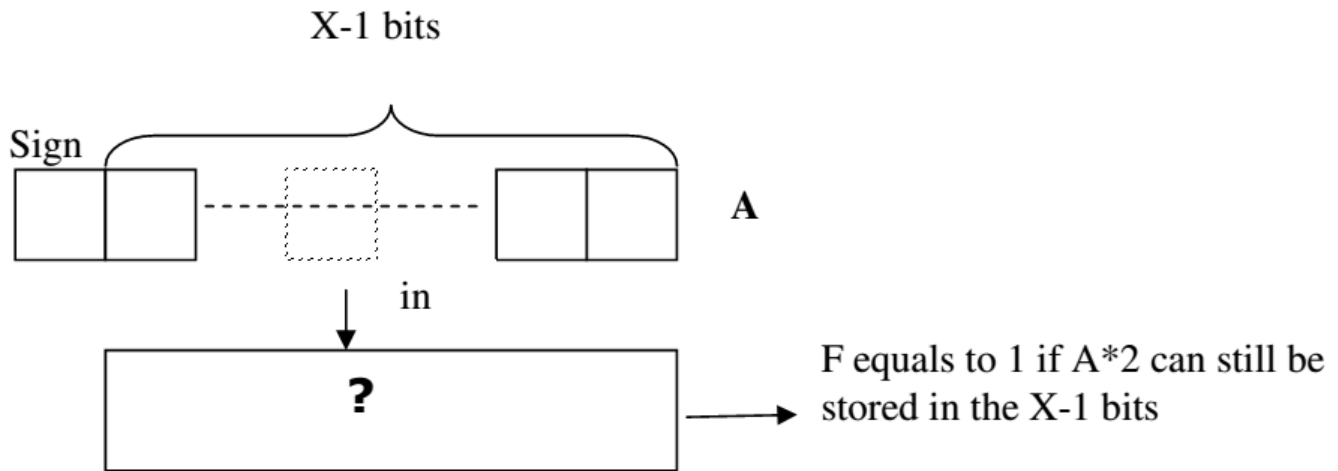

**Figure 1**

**2:** Obtain the minimal Sum of Products expression for function  $F(A, B, C, D) = \sum(4, 5, 6, 7, 8, 9, 10, 11)$  using Quine McCleskey method. [5]

**3:** Design a counter that uses JK flip flops and goes through the following repeated sequence: 0, 1, 2, 4, 5. (Treat the unused states as don't care conditions).

a. Show the state diagram

b. Design the circuit using the minimum number of 2-input gates.

d. If by mistake (e.g., interference) your circuit jumps to number 3, is it still going to work? Explain. (Hint: show what happens if your circuit has state 011) [1 + 3 + 1].