

# Digital Circuits and Systems

## Mid Semester Exam

Date: 3<sup>rd</sup> Sep. 2013

Time: 55 Minutes

Max Marks. 30


Notes: All questions are compulsory.

Marks of each question are mention against it.


Assumptions made should be written clearly.

**1:** Analyze the circuit given in figure 1 and express the value of **f** in OAI form.

[5]

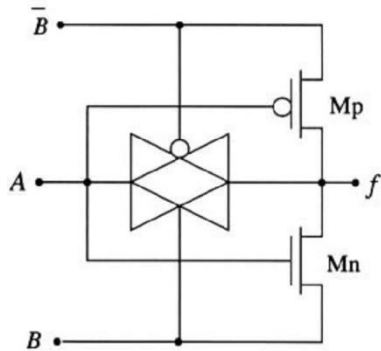

**Figure 1**

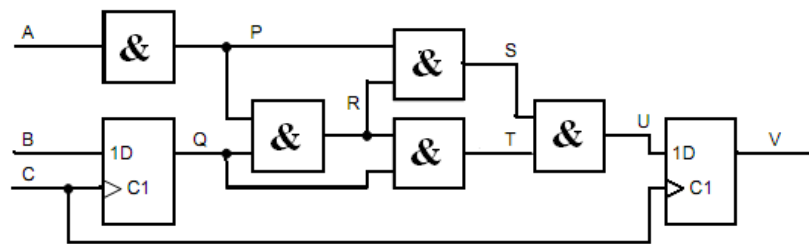

**Figure 2**

**2:** Implement the function  $Z = F(A, B, C) = \sum m(1, 3, 6)$  using only one PFET and multiple NFETs.

[5]

**3:** Describe a 2x2 bits multiplier, that is, each operand represents an integer in the range 0 to 3. Give the following descriptions.

High level using arithmetic expressions.

Table of arithmetic functions

A table representation of switching functions, with inputs and outputs in a binary code.

[5]

**4:** Consider the following system description.

Input:  $x(t) \in \{0,1\}$

Output:  $z(t) \in \{0,1\}$

Function:  $z(t) = \begin{cases} 1 & \text{if } x(t-2, t) = 101 \\ 0 & \text{otherwise} \end{cases}$

If input sequence from  $t=0$  to  $t=8$  is 001010100 Then what is the output sequence.

[5]

**5:** In the circuit shown in figure 2, the propagation delay of the flip flops may vary between 4 and 7 ns while the propagation delay of the gates may vary between 2 and 6 ns. Calculate the minimum and the maximum propagation delays between C and U. Hence calculate the maximum frequency of the clock, C.

[5]

**6:**

(A) If a system has inputs from decimal numbers 5 to 20, how many minimum binary bits are required to describe the system in binary?

[2]

(B) A combinational system has as input a 3 digit decimal number and as output the 9's complement of the system. Give a high level description of the system.

[3]