

Electronics II
Mid Semester Exam II

Date: 13th March 2014

Time: 60 Minutes

Max Marks. 30

Notes: If not mentioned, then you can ignore I_B in problem solving.

Marks of each question are mention against it.

Assumptions made should be written clearly.

-
- 1:** For the circuit given in figure 1, find out R_E , R_C , R_B , V_E , and V_C . [5]
- 2:** Design a common emitter voltage divider biased amplifier with $V_{CC} = 20V$, $I_C = 10mA$, $\beta = 100$ and Q point is at the centre. [5]
- 3:** In the Common base amplifier given in figure 2, find out I_E , V_C , V_E , A_v , Z_i , Z_o and A_{vs} . Also plot the input voltage graph at emitter and output voltage at collector. (Both AC and DC voltages are to be considered in the waveform.) [7 +3]
- 4:** For cascaded amplifier given in Figure 3, find out A_{v1} , A_{v2} (Voltage gains of each stage with load), A_{vT} (total gain of the system w.r.t v_i) and v_o . [5]
- 5:** For the circuit given in figure 4, find out the values of I_C , I_B , V_C and V_E . [5]