

The LNM Institute of Information Technology, Jaipur
Department of Electronics and Communication Engineering
Engineering Electromagnetics (ECE 335)

Exam Type: Quiz
Degree*: B.Tech
Time : 60 minutes


Academic Year: 2017-18
Programme*: B.Tech in ECE
Date: 19/09/2017

Semester: ODD
Year: 2nd and 3rd
Maximum Marks: 30

	CO1	CO2	CO3	CO4	CO5
Questions	1,2a	3,4	-	-	-
Marks	6+2	22	-	-	-
Marks/Max Marks (%)	27	73	-	-	-

Instruction: Write answer to all parts of question in same place. Write Roll no on top right corner of the smith chart.

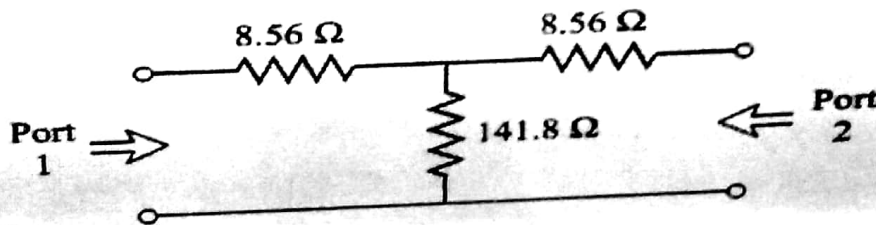[Q1]. Find the scattering parameters of the 3 dB attenuator with characteristic impedance 50Ω circuit shown in figure below. Also find Z_{11}




[2+2+2=6]

[Q2]. A telephone line operated at 1 kHz has $R = 30 \Omega/\text{km}$, $L = 100 \text{ mH}/\text{km}$, $G = 0$, and $C = 20 \mu\text{F}/\text{km}$. obtain

- (a) The value of α in dB/km.
- (b) The characteristic impedance of the line.

[2+2=4]

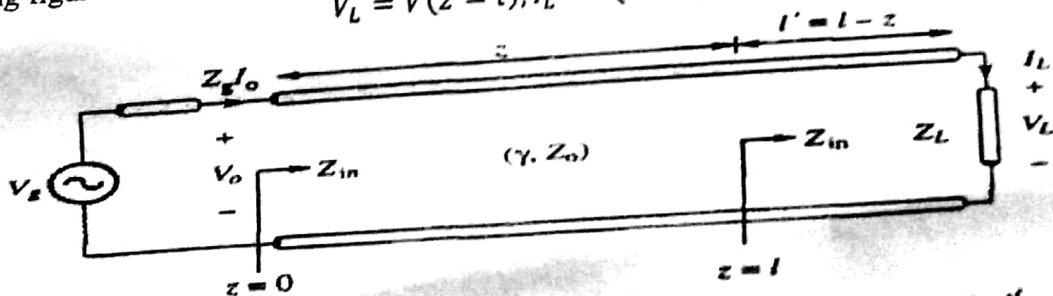[Q3]. (a) In the following figure derive equations for V_0^+ and V_0^- . Given the conditions at the load $V_L = V(z=l)$, $I_L = I(z=l)$



(b) Show that the voltage reflection coefficient at any point on the line is given by $\Gamma(z) = \Gamma_L e^{-2\gamma l'}$

[4+4=8]

[Q4]. A 30-m- long transmission line with $Z_0 = 50 \Omega$ operating at 2 MHz is terminated with a load $Z_L = 60 + j40 \Omega$. If the velocity of propagation on the line is $u = 0.6c$, find with and without using Smith Chart

- (a) The reflection coefficient Γ
- (b) The standing Wave Ratio S
- (c) The input impedance.

Use different color to indicate clearly the impedance and admittance. Label points.

[(2+2+2)+(2+2+2)=12]

(5)