

The LNM Institute of Information Technology

Department: ECE
 Basic Electronics (ECE103)
 Exam Type: Mid Term

Time: 90 minutes

Date: 25/09/2019

Max. Marks: 30

- Instructions:** 1. This question paper consists of 3 printed pages.
 2. All the questions are compulsory.
 3. Attempt each new question in a fresh page.
 4. Clearly mark all the answers with a box or underline.

- Q.1** a) In the circuit shown below (Fig. 1a), find the total resistance R_T , with terminals a and b : i) open circuited ii) short circuited. [2]

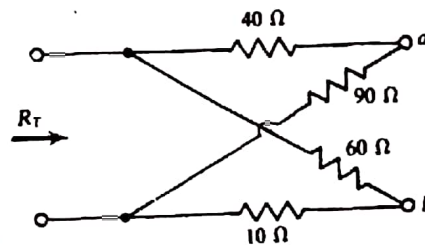


Fig. 1a

- b) In the interval $0 > t > 5\pi$ ms, a 20-mF capacitance has a voltage $v = 50.0\sin 200t$ (V). Obtain the charge, power, and energy. Plot energy (w_c) assuming $w = 0$ at $t = 0$. [3]

- Q.2** a) In the circuit shown below (Fig. 2a), find the resistance R_{ab} , with the value of each resistance being 30Ω . [2]

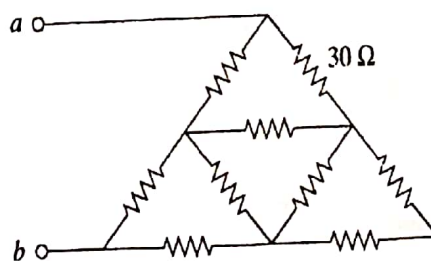


Fig. 2a

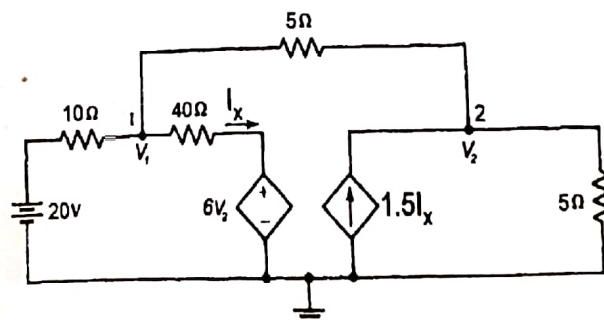


Fig. 2b

- b) Obtain voltages V_1 and V_2 given in the circuit shown in (Fig. 2b). [3]

- Q.3 a) In the circuit shown below (Fig. 3a), find the Thevenin's equivalent V_{th} and R_{th} to the left of terminals a and b (in terms of V_{in}). Also calculate the transfer resistance $R_{transfer} = V_{in}/I_4$ in terms of R_L when R_L is connected. [3]

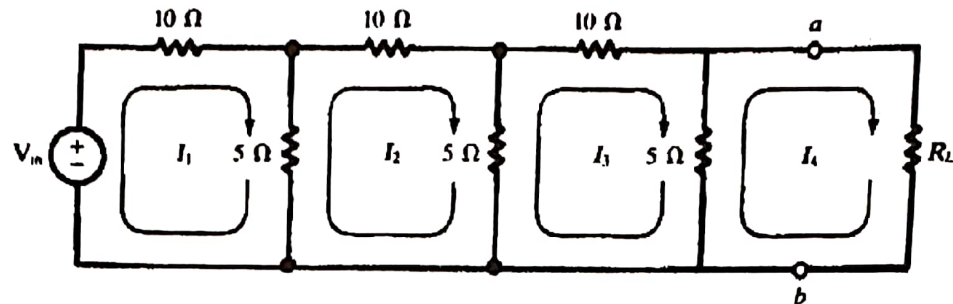


Fig. 3a

- b) Find the value of the adjustable resistance R which results in maximum power transfer across the terminals ab for the circuit shown in Fig. 3b. Also determine the value of the maximum power P_{max} . [2]

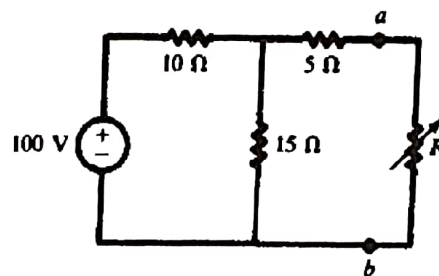


Fig. 3b

- Q.4 a) In the circuit shown in Fig. 4a, the initial voltages across the capacitors C_1 and C_2 are 1V and 3V respectively. The switch is closed at time $t=0$. How much energy will be dissipated (in Joules) in the resistor R until the steady state is reached. [3]

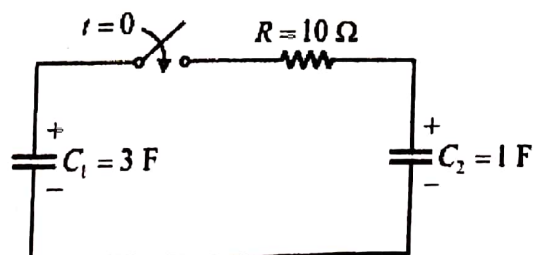


Fig. 4a

- b) In the given circuit **Fig. 4b**, the switch S is closed at $t = 0$. Derive the expression for the rate of change of current $\frac{di(t)}{dt}$ at $t=0^+$. [2]

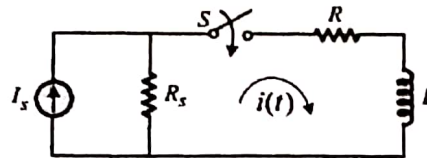


Fig. 4b

- Q5. a) The responses of a series RLC circuit are: [3]

$$v_C(t) = 30 - 10e^{-20t} + 30e^{-10t} \text{ V}$$

$$i_L(t) = 40e^{-20t} - 60e^{-10t} \text{ mA}$$

where v_C is the capacitor voltage and i_L is the inductor current. Calculate the value of R , L and C .

- b) For the circuit shown in **Fig. 5b**, the switch is closed for a long time and opens at $t=0$. Find the response of the system and voltage across capacitor as a function of time for $t > 0$. [2]

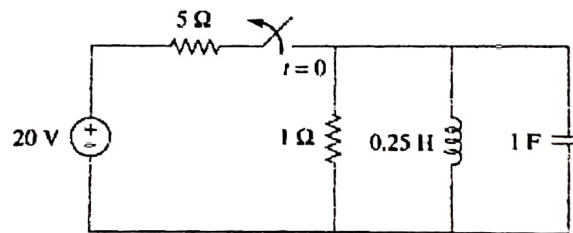


Fig. 5b

- Q6. a) For the circuit shown **Fig. 6a**, the switch is closed at $t=0$. Find response of the system and $i(t)$ for $t > 0$. [3]

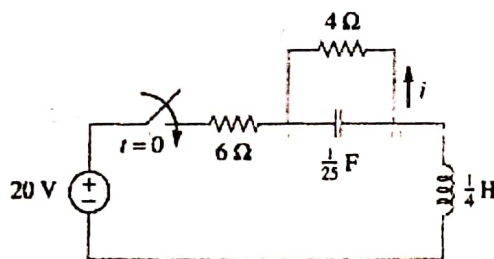


Fig. 6a

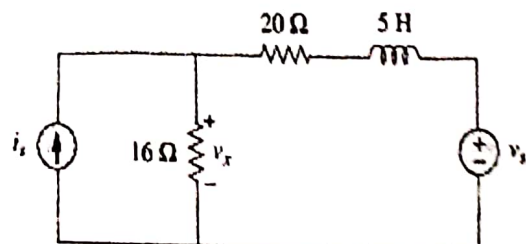


Fig. 6b

- b) Using superposition principle, calculate V_x in the circuit shown in **Fig. 6b** if $v_s = 50 \sin 2t \text{ V}$ and $i_s = 12 \cos(6t + 10^\circ) \text{ A}$. [2]