

The LNM Institute of Information Technology, Jaipur
Electronics and Communication Engineering Department

Engineering Electromagnetics(ECE335)

Exam Type: Mid Term
Degree: B.Tech

Academic Year: 2017-18 Semester: ODD
Programme: ECE Year: 2nd and 3rd

Time : 90 minutes

Date:28/09/2017

Full Marks: 50

	CO1	CO2	CO3	CO4	CO5
Questions	1,2,5a	3,4,5b,5c,6	-	-	-
Marks	20	30	-	-	-
Marks/Max Marks (%)	40	60	-	-	-

Instruction: No query will be entertained during examination. If you think any data is missing, assume suitable values. Write answer to all parts of question in same place. Write Roll no on top right corner of the smith chart. You can solve question by Smith Chart also.

[Q1]. (a) In the following circuit interconnection between Two Port Networks T_1 and T_2 is shown Find ratio between V_1 and V_2 .

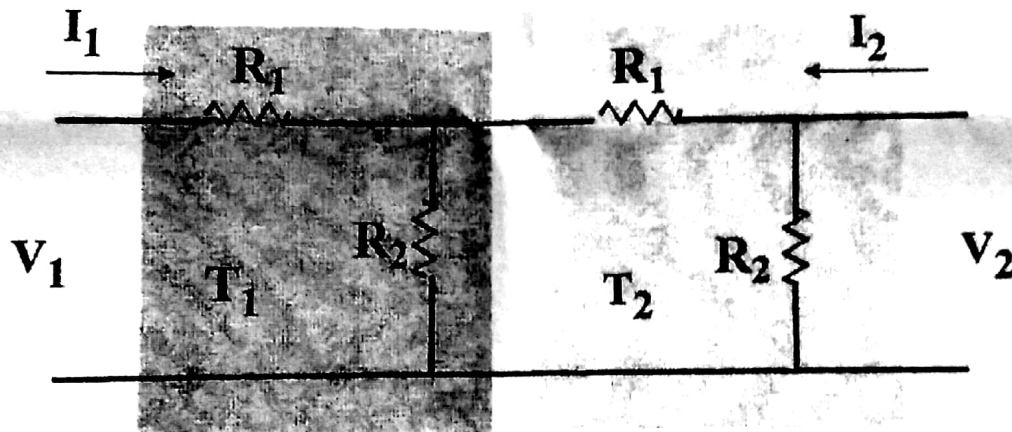


Figure 1. Cascaded Two Port Network

(b) Given Z_0 equal to 50Ω , find S_{11} and S_{22} for the circuit given in figure 2.

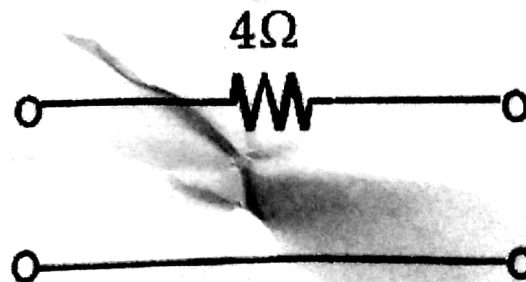



Figure 2. Circuit for question 1b

[3+3+2+2=10]

[Q2]. (a) A signal with power 3mW is distorted by noise with power -30dBm. What is the signal to noise Ratio(SNR) in dB.

(b) Prove that Noise Figure of a system as represented in following figure is given by,

$$F = \left(1 + \frac{T_e}{T_{in}} \right) \Big|_{T_{in}=290K}$$

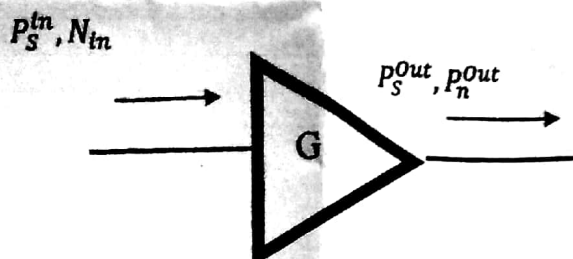

[2+3+3=8]

[Q3]. (a) In the circuit given in figure 3, calculate maximum power output from source with impedance Z_S that can be absorbed into load.

(b) The power flow into a one-port circuit can be written in the following form $P_{in} = P_{AVS} - P_r$, where P_{AVS} is the available power from the source. Assume source is sinusoidal and in steady state. If the source has a real resistance Z_0 and it emitting complex power, then show that

$$P_r = P_{avs} \left| \frac{Z_{in} - Z_0}{Z_{in} + Z_0} \right|^2$$

(c) If $P_{AVS} = P_{Load}$, find S_{11} for the circuit in figure 3.


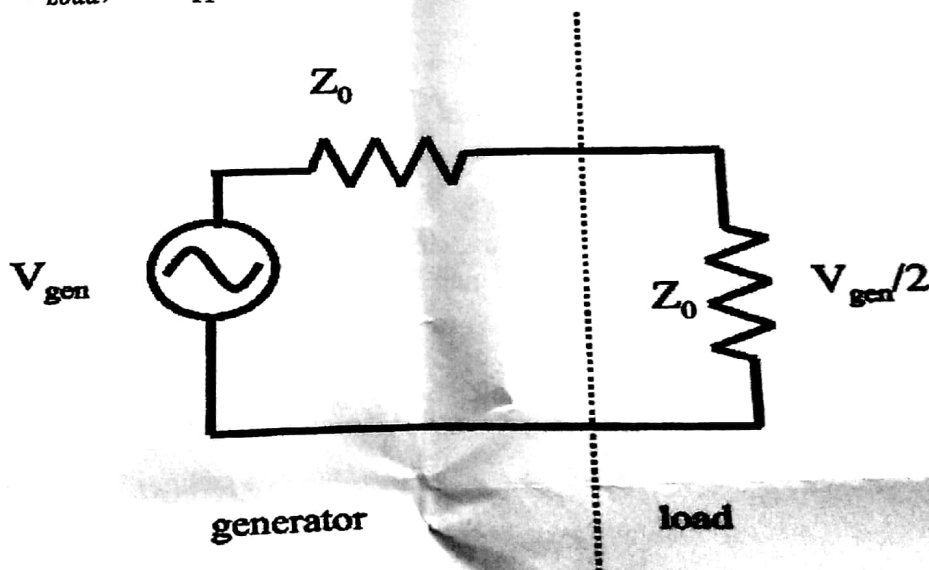


Figure 3. Circuit for Question 3.

[2+2+2=6]

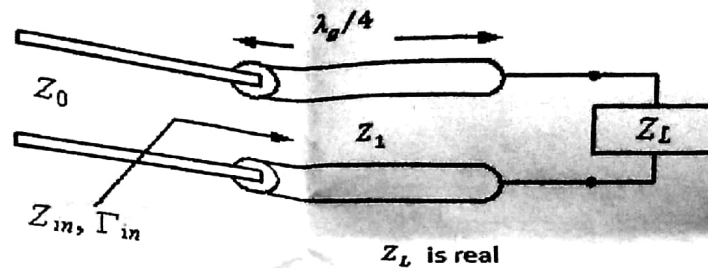- [Q4]. (a) Derive the input impedance formula for a lossless transmission line.
(b) Find the input impedance for the transmission line given below.



- (c) A unknown load connected to a slotted air line, produces a SWR, $S=2$ by the standing wave indicator and minimas are found at 14cm, 22cm, 30 cm. on the scale. when the load is replaced by a short circuit, the minimas are at 19cm, 27cm, 35cm .. If Z_0 is 50Ω , calculate the value of Z_L .

[4+3+3=10]

- [Q5]. The input impedance of a short-circuited lossy transmission line of length 1.5 m ($< \lambda/2$) and a characteristic impedance of 100Ω (approximately real) is $40 - j280 \Omega$.

- (a) Find α and β of the line.

- (b) Determine the input impedance if the short-circuit is replaced by a load resistance


$$Z_L = 50 + j50 \Omega.$$

- (c) Find the input impedance of the short-circuited line for a line length of 0.15λ .

[2+2+2=6]

- [Q6.] Consider the lossless transmission line network shown below. The operating frequency is 2000 MHz and the propagation velocity on the transmission line is 0.3 m/ns.

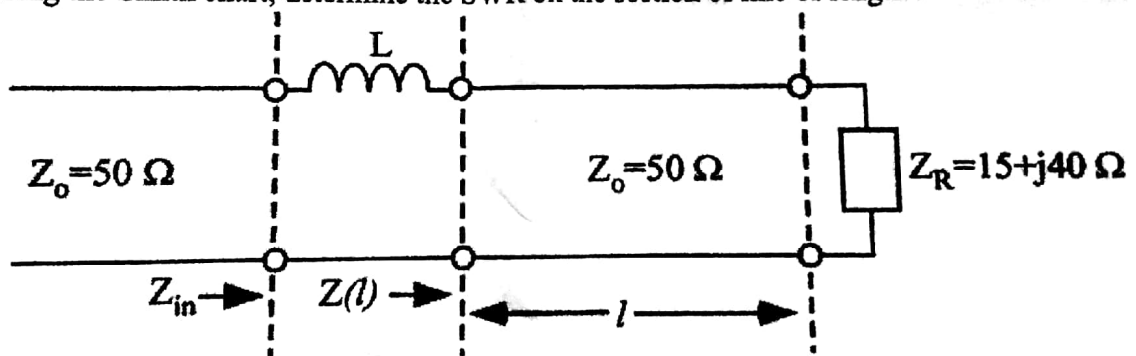- (a) Using the Smith chart, determine the SWR on the section of line of length l



- (b) Using the Smith chart find two values for the length l such that $Z(l)$ is equal to $Z_0 \pm jX$.

- (c) Determine the value of series inductance L and the proper length of the transmission line section (l_1 or l_2) that insures $Z_{in} = Z_0$

- (d) Match a load impedance $Z_L = (100 + j80) - \Omega$ to a line with characteristic impedance $Z_0 = 75 - \Omega$ using a shunt single-stub tuner. Find solution using a short-circuited stub.

[2+2+2+4=10]