

Electronics I

Lab Written Test

Name:

Roll No:

Section:

Date: 4th November 2016

Time: 60 Minutes

Max Marks. 30

Notes: All questions are compulsory and each question carries 1 mark.

Assumptions made/clarifications should be written clearly.

1. CRO is an analog or Digital instrument?

Analog

2. Mention the colour sequence of rings for 85k Ω resistor with 5% tolerance and having 4 rings?

Gray, Green, Orange, Gold

3. What is the minimum voltage/division in the CRO present in the lab?

5 mV

4. What is the power rating of for most of the common resistors in our lab?

0.25 W

5. Why do we use bulky (power) resistor for few of the experiments?

If the power absorbed by the resistor would be more than 0.25W.

→ This protects the circuit from blowing because of excessive heat

6. What is the purpose of X-Y mode in CRO?

To get Lissajous figure for a component. For capacitor, it is circle, and ellipse for RC.

7. What is written on the body of 10nF ceramic capacitor?

103

8. If you have four 1k Ω resistors in parallel and one of them is blown, then what is the effective resistance offered by the combination?

Now we have 3 resistors in parallel.

$$\therefore R_{eff} = 333 \Omega$$

9. If three different resistors are placed in series with a voltage source, which resistor have the greatest power loss?

The one with highest resistance
 \therefore each will have equal current.


$$\text{and } P = I^2 R$$

10. Typical Resistance of Voltmeter should be:

$$\text{Ideal} = \infty$$

$$\text{Typical} \leftarrow 50k\Omega \gg 100M\Omega$$

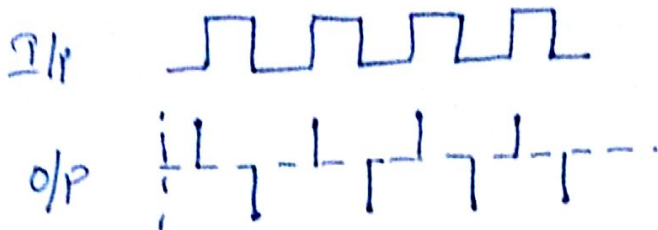11. When a square pulse is given as input to Op-Amp differentiator, draw the input and output waveforms.



12. In an Op-Amp integrator what combination of R and C will make sure that input and output signals have same amplitude?

Product of R and C should be 1.

$$\text{or } R = 1/C$$

13. Minimum number of bits required to represent binary numbers 31 to 45 are?

Total numbers to be represented are 15

$$\therefore \text{Min bits} = 4$$

14. A system have 3 inputs (x, y, z) and one output (P). P is '1' if there are more number of 1's in the input vector. Write down the truth table to representing this system.

x	y	z	P
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

15. Find out the Optimized SoP for Question. 14

P	yz=00	01	11	10
x				
0			1	
1		1	1	1

$$P = xy + yz + xz$$

16. Obtain the Maxterms of the function $f(A,B,C) = (A+B)C$

$$= AC + BC$$

A	BC=00	01	11	10
0	0	0	1	0
1	0	0	1	1

\therefore Maxterms are (0, 1, 2, 4, 5)
or

$$(A+B+C), (A+B+\bar{C}), (A+\bar{B}+C)$$

$$(\bar{A}+B+C) \text{ and } (\bar{A}+B+\bar{C})$$

17. If you have Norton equivalent of a circuit, then how to find the Thevenin equivalent of the same?

By I_{NO} and R_{NO} make Norton equivalent.


Then series combination of R_{NO} and $V_{TH} = (I_{NO} \times R_{NO})$ is Thevenin equivalent.

18. Convert $(348A)_{16}$ into quaternary number system (base = 4)

$$(348A)_{16} = (0011, 0100, 1000, 1010)_2$$

$$= (03102022)_4$$

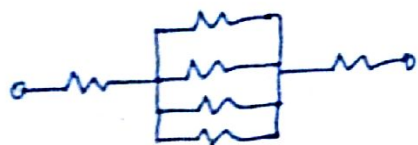19. You have only 100Ω resistors with you. How would you obtain 225Ω using minimum number of such transistors?



each $R = 100\Omega$.

20. Why can't we measure current in parallel?

\because Ammeter have ~~infinite~~ ^{zero} resistance and thus all the current will flow through it and none through the element.

21. How can we improve power factor of an inductive load (like AC motor)?

By connecting a Capacitor in parallel to the load.

22. Why can't the output of Op-Amp be less than $-V_{CC}$?

\because The internal BJT's can't produce an output below the minimum voltage supplied which is $-V_{CC}$.

23. Define Superposition Theorem.

Theorem states that, for a linear system, the response in any branch is algebraic sum of responses caused by all independent sources present in the circuit.

24. Define Super-node.

In KCL super node represents a surface, in which ~~can be~~ all the nodes can be represented by a single variable along with some constant values.


25. What does Bode plot show?

Bode plot represents the frequency response of a circuit.

It's a plot of Amplitude/gain Vs frequency.

26. The cut off frequencies of a Band stop filter are f_{HPF} and f_{LPF} which one is higher?

f_{HPF} would be higher

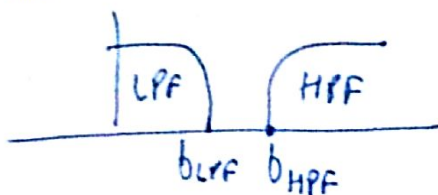

27. How to calculate the energy stored in an inductor?

$$E = \frac{1}{2} L I^2$$

28. Define active and passive elements in a circuit.

Passive Elements: Those components which don't generate power, but dissipate, store/release it.
(R, L, C)

Active Elements: Those components which generate power.

29. What is the average value of a pure sinusoidal wave with peak amplitude 10V, and frequency 10 kHz.

Avg Value = 0.

30. Write the names of lab superintendent, 1 faculty member and 4 TAs associated with the lab.

Lab Superintendent: Kushmala Sharma

FACULTY MEMBER:

NIKHIL SHARMA, JOYEETA SINGHA
SOVAN MUKHERJEE, SANTOSH SHAH

TAs.

1. Shobhit Agarwal

2. MONIKA JAIN

3. Vaidehi Sharma

4. Mohita Jaiswal

5. Saurabh Soni

6. Samyaks Dutt Gupta

7. Shourya Shubham

8. Kritika Johari

9. Himanshu Jain

10. Ruchi Gupta

11. Harshit Somani

12. Shriya Rai

13. Meenakshi Modi

14. Mithun Nair

15. Anusha Agarwal

16. Ankit Puri

17. Aarsha Bhargava

18. Deepa Daga

19. Bharti Sharma

20. Himanshi Khandelwal

21. Ridhii Gupta

22. Nishita Gupta

23. Shivansh Bhattacharya

24. Shiwani Manhas

25. Pooja Singh Jain

26. Sparsh Datta

27. Samyans Jain

28. Saumya Mishra

29. Deeksha Gupta