

**Electronics II**  
**End Semester Exam**

**Date: 28<sup>th</sup> April 2014**

**Time: 180 Minutes**

**Max Marks. 50**

---

**Notes: If not mentioned, then you can ignore  $I_B$  in problem solving.**

**If not mentioned, use first approximation for diodes.**

**Assumptions made should be written clearly.**

---

Q.1: Draw the output waveform of following 3 circuits Consider a sine wave of amplitude 5V as input and plot the output waveform for 2 cycles. Consider Ideal diodes for all 3 figures. [3 + 3+ 4]

Q.2: Analyze the circuit given in figure 4 and find out  $I_C$ ,  $V_E$ ,  $V_{CC}$ ,  $V_{CE}$  and  $R_1$ . [5]

Q.3: Analyze the circuit given in figure 5 and find out the value of 3dB Bandwidth of Amplifier. Consider  $\beta = 100$ ,  $C_{BC} = C_{BE} = 10\text{pF}$ . [10]

Q.4: Design a Wein Bridge Oscillator. What is the value of attenuating and amplifying factors in this oscillator? [5]

Q.5: Design a pulse width modulator using NE555. If  $R = 2\text{k}\Omega$ ,  $C = 5\text{nF}$  and  $V_{CC} = 12\text{V}$  then find out the minimum and maximum width that can be produced by this modulator. Also write down a suitable frequency of the triggering pulse. [5]

Q.6: Analyze the circuit given in figure 6 and find out the value of  $V_{out}$ ,  $I_{out}$  and power dissipated in the circuit. [5]

Q.7: For a 6 bit Flash ADC with  $V_{ref} = 5V$ , find the thermometer code for input voltages 1.621 and 3.778V. Also find the corresponding Binary codes.

Q.8: Design a 3 bit R-2r Ladder DAC circuit. [3+2]

Q.9: Design electronics TOSS circuit. The circuit should show output in the form of a glowing LED, either Red or Green. Once a switch, named 'TOSS' is pressed and then released after sometime then only one of the LED should remain on and other should be off. [5]